

[illegible]

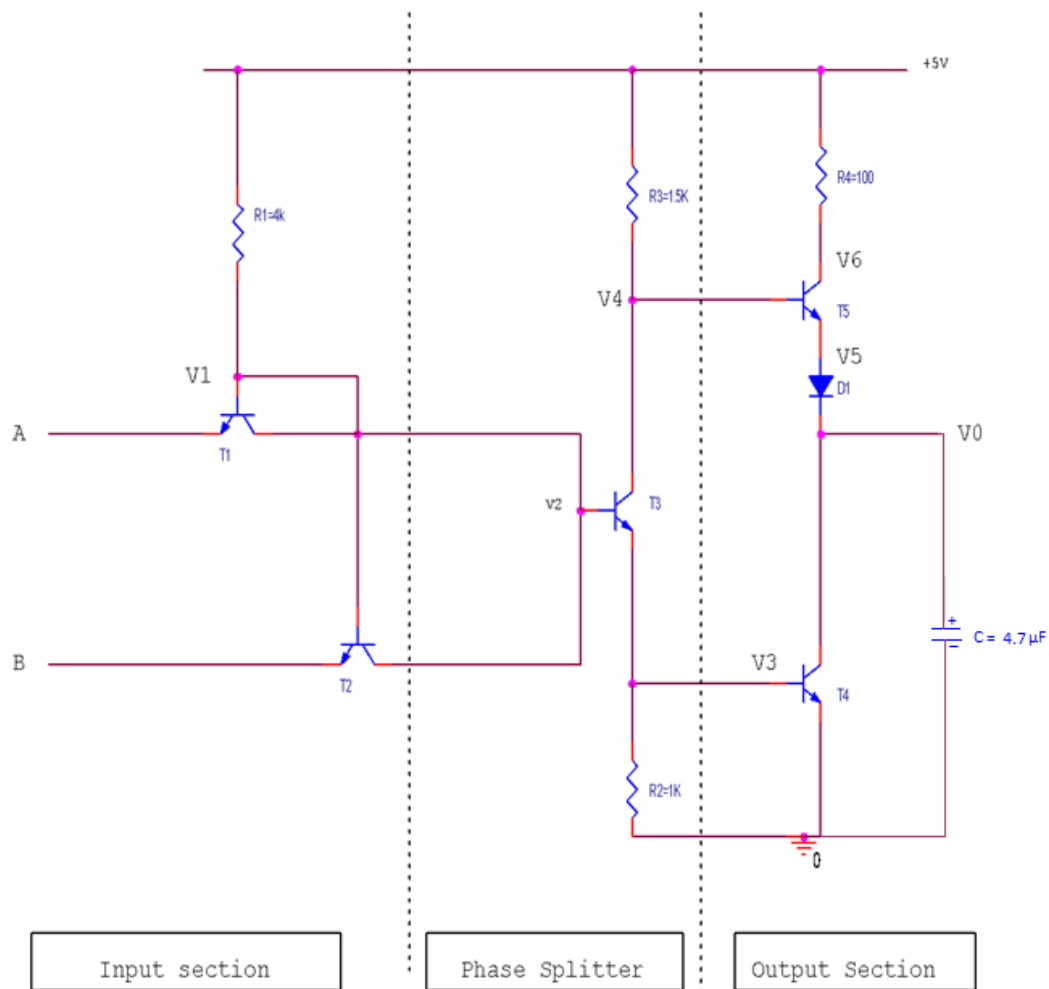


Figure 1: TTL NAND gate with Totem Pole output

Report

1. What is totem pole stage?
2. Why is totem pole used in place of a passive pull up resistor?
3. What is the function of T3(phase splitter)?
4. What may happen if diode D1 is not used in the circuit?
5. What is the mode of operation of the T5 transistor when output is high?
6. Draw the active portion of the circuit when output is low.
7. Design a TTL NOR gate with Totem Pole Output Stage.

Reference

Reference: Microelectronics: Digital and Analog Circuits and Systems by Jacob Millman