

Experiment-05

CSE 350

Group - 01

Section - 1

Submitted By -

Ishraq Ahmed Esha

ID: 19301261

Report

Experiment Name: Analysis of triangular wave Generators.

Objective: The objective of this experiment is to analyze a bipolar and unipolar triangular wave generator.

Equipments: (1) Trainers board

(2) 741 opamp

(3) Resistors: $10k\Omega$ - 2 units

$4k\Omega$ - 1 unit

(4) Capacitor - $0.05/0.4\mu F$ 1 unit.


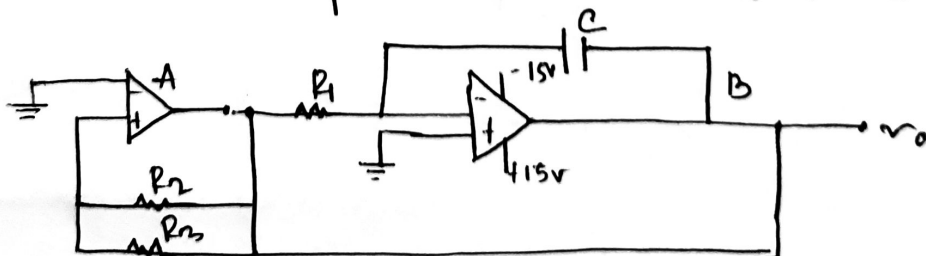


Fig: circuit diagram.

Electric current flows through the capacitor through R_1 , when A is positive. Voltages at both end of the capacitor goes up, when the voltage of the point B falls gradually. The point C breaks up the voltage difference between A and B, with resistor R_1 and R_2 . Voltage of point C also goes down as voltage of Point B goes down, when the voltage of point C falls down below zero, the voltage of point A changes into minus. The condition of $R_2 \gg R_1$ is necessary for voltage fall below 0V. Thus, causes current of capacitor to reverse. The current now flows through the direction of A through R_1 , with this the voltage of point C gradually rises, when the voltage of C gradually rises, the output of point A changes to positive, changing the point B to the direction of the negative. And the process repeats

Integrator circuit using Inductor.

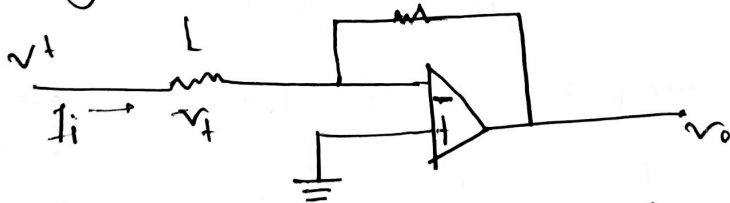

$V^- = v_i = 0V$ Grounded virtual short cir.
opamp ideal; current through $= 0A$.

Current through resistor $R = \frac{0 - v_o}{R} = -\frac{v_o}{R}$ — (1)
Apply KCL to P.

$$I_L = 0 + I \quad I = I_L \quad \text{--- (2)}$$

Apply KVL

voltage across Resistor

$$v_L = v_i = 0$$

$$v_L = v_i \text{ --- (3)}$$

Inductor voltage given by,

$$v_L = L \frac{di_L}{dt}$$

From (1) and (2)

$$v_L = L \frac{di_L}{dt} = L \frac{d(-v_o/k)}{dt}$$

$$\therefore v_L = -\frac{L}{R} \frac{dv_o}{dt}$$

from (3) we have,

$$v_i = -\frac{L}{R} \frac{dv_o}{dt}$$

$$\text{or, } \frac{dv_o}{dt} = -\frac{R}{L} v_i$$

$$\therefore dv_o = -\frac{R}{L} v_i dt$$


Integrating both side:

$$\int dv_o = -\int \frac{R}{L} v_i dt$$

$$\therefore v_o = v_o = -\frac{R}{L} \int v_i dt + C$$

$k = \text{constant}$

Report

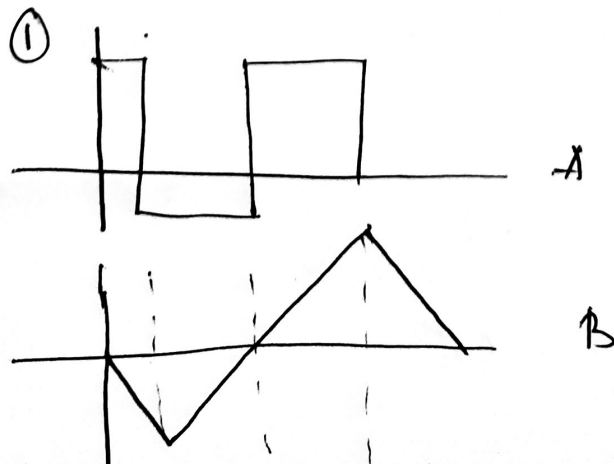

$$F = \frac{1}{4 \times 10 \times 10 \times 4 \times 10^{-6}} \times \frac{10}{4}$$

$$= 156.25 \text{ Hz}$$

Theoretical freq.	Experimental Time Period	Experimental freq
156.25 Hz	7.7 ms	130.9 Hz

$$F = \frac{1}{4 \times 10 \times 0.4 \times 10^{-6}} \times \frac{10}{4}$$

~~$$= 156.25 \text{ Hz}$$~~

$$= 156.25 \text{ Hz}$$

Theoretical Frequency	Experimental Time Period	Experimental Frequency
156.25 Hz	7.7 ms	130.9 Hz

Shimant
31/7/22